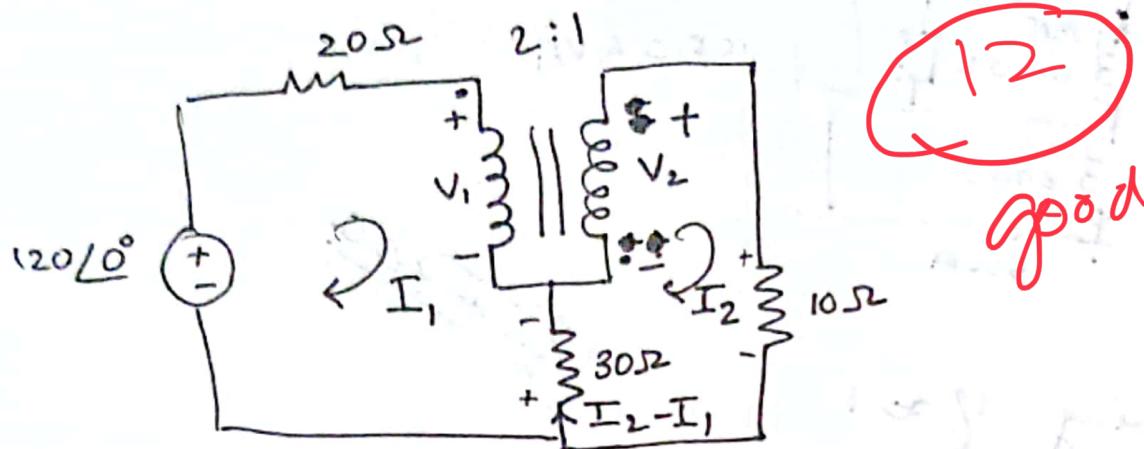


Quiz

19D170027
Sanidhya



12
good

Applying KVL

$$120\angle 0^\circ - 20I_1 - V_1 - 30(I_2 - I_1) = 0 \quad \text{---} \textcircled{1}$$

Applying KVL

Check or

$$-V_2 - 10I_2 - 30(I_2 - I_1) = 0 \quad \text{---} \textcircled{2}$$

And,

$$\frac{V_1}{-V_2} = \frac{2}{1} \quad \checkmark \quad \text{and} \quad \frac{I_1}{I_2} = \frac{1}{2}$$

$$\Rightarrow V_1 = 2V_2 \quad \Rightarrow 2I_1 = I_2$$

Substituting in ①

$$120\angle 0^\circ - 20I_1 + 2V_2 - 30(I_1) = 0$$

$$\Rightarrow 120\angle 0^\circ = 50I_1 + 2V_2$$

Substituting in ②

$$-V_2 - 10I_1 - 30(I_1) = 0$$

$$\Rightarrow V_2 = 50I_1$$


$$\therefore 120 = V_2 - 2V_2 \quad \textcircled{2}$$
$$\Rightarrow V_2 = -120 \text{ V}$$

$$\therefore V_1 = 240 \text{ V}$$

$$\Rightarrow I_1 = \frac{V_2}{50} = -2.4 \text{ A}$$

$$I_2 = 2I_1 = -4.8 \text{ A}$$
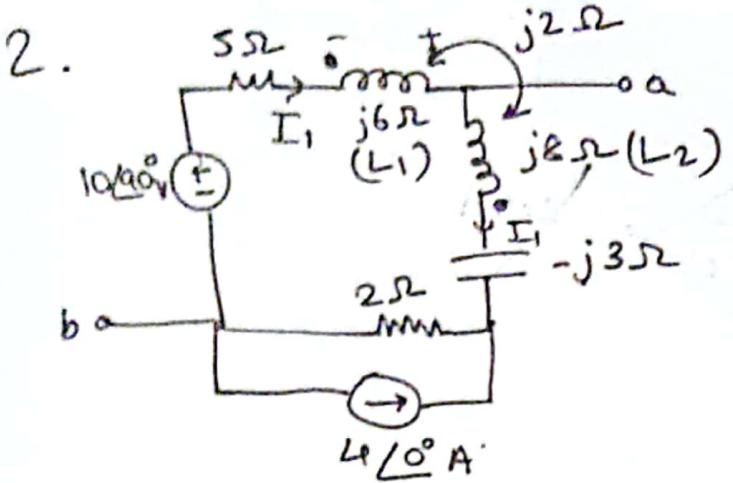
$$P_{10\Omega} = I_2^2 R$$
$$= 4.8^2 \times 10 = 23.04 \times 10$$
$$= 230.4 \text{ W}$$




For R_{th}

$$\begin{aligned} L_1' &= L_1 - j2\Omega \\ &= j6 - j^2 \\ &= j4\Omega \end{aligned}$$

$$\begin{aligned} L_2' &= L_2 - j2\Omega \\ &= j8 - j^2 \\ &= j6\Omega \end{aligned}$$

$$\therefore L_1' + L_2' = j4 + j6$$



Redrawing

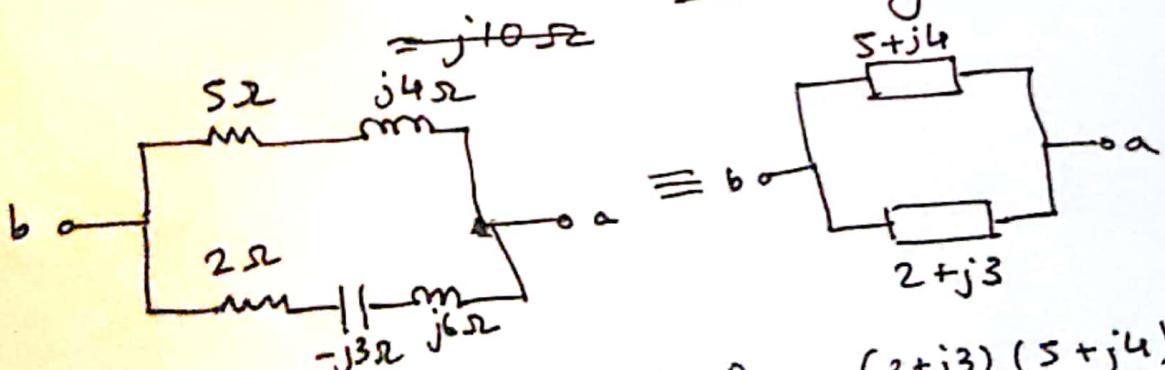

$$\Rightarrow R_{th} = \frac{(2+j3)(5+j4)}{7+j7}$$

$$= 2.33 \cancel{149.97^\circ} \Omega$$

For V_{th}

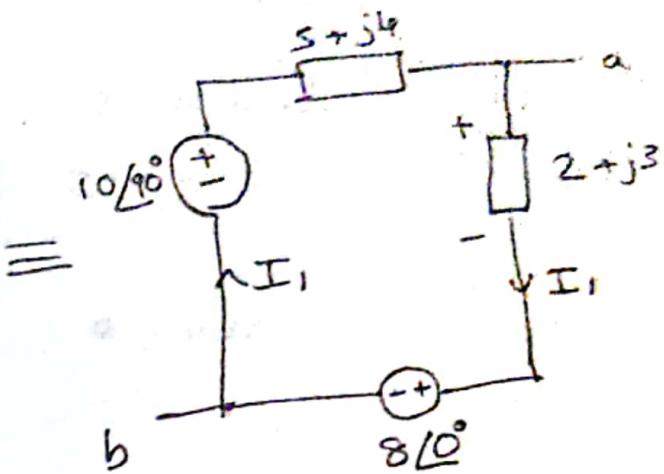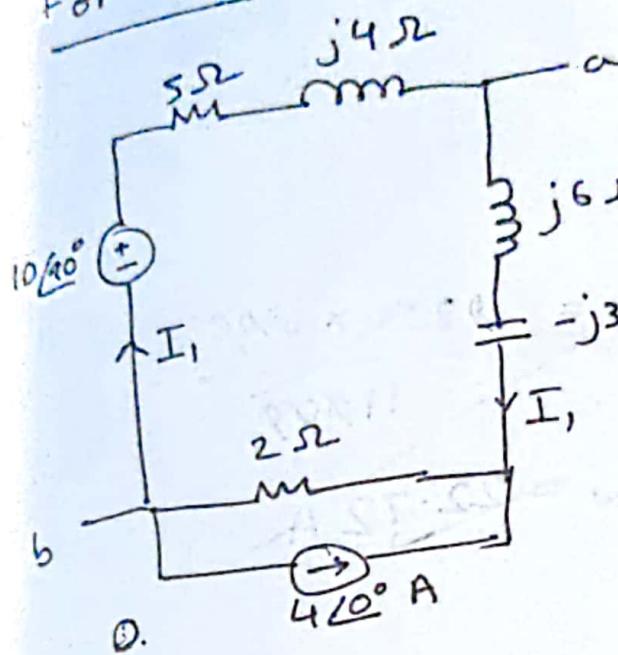

(H)

∴ Applying KVL

$$+10\angle 90^\circ - I_1(S+j4) - I_1(2+j3) - 8\angle 0^\circ = 0$$

$$\Rightarrow 10\angle 90^\circ - 8 = I_1(7+j7)$$


$$\Rightarrow I_1 = 1.29 \angle 83.66^\circ \text{ A}$$

$$\therefore V_{ab} = (2+j3)I_1 + 8\angle 0^\circ$$

$$= 3.6 \angle 56.31^\circ + 1.29 \angle 83.66^\circ + 8\angle 0^\circ$$

~~$$V_{ab} = 5.35 \angle 33.91^\circ$$~~
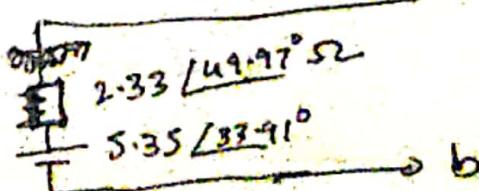
$$V_{ab} = 5.35 \angle 33.91^\circ = V_{th}$$



Thévenin
equivalent

∴

$$3. X = 100 \text{ kVA}$$

$$\Rightarrow \text{Power rating} = 150 + X \\ = 250 \text{ kVA}$$

rated current \propto : $I_{\text{HV}} = \frac{250 \times 1000}{11000 \phi}$
 $I_{\text{HV}} = 22.72 \text{ A}$

$$P = \sqrt{3} V_L I_L$$

$$V_L = 11000 \text{ V (Delta)}$$

(i)

$$\therefore 250 \times 1000 = \sqrt{3} \times 11000 \times I_L$$

$$I_{\text{HV rated}} = 13.14 \text{ A}$$

$$\therefore P_{\text{CL}} = \frac{I_{\text{HV rated}}^2}{3} R_{\text{eq2}} \times 3 \quad (\text{as } I_p = \frac{I_L}{\sqrt{3}})$$

3 resistances

$$\Rightarrow R_{\text{eq2}} = \frac{2.1 \times 1000}{13.14^2 \times 3}$$

$$R_{\text{eq2}} = 12.16 \Omega \quad 2$$

$$Z_{\text{eq2}} = \frac{350}{13.14} = 26.64 \Omega \quad Y$$

$$\therefore X_{\text{eq2}} = \sqrt{Z_{\text{eq2}}^2 - R_{\text{eq2}}^2} = 23.70 \Omega \quad Y$$

$$P_{OC} = 3 \times \frac{400^2}{R_{CL}}$$

$$\Rightarrow R_{CL} = 3 \times \frac{400 \times 400}{1500}$$

$$R_{CL} = 320 \Omega$$

$$\Rightarrow I_c = \frac{400}{320} = 1.25 A$$


$$\text{Now, } I_x = \sqrt{I_i^2 - I_{cL}^2}$$

$$= \sqrt{9^2 - 1.25^2} = 8.91 A$$


$$\gamma = \frac{3 \times 250 \times 1000}{3 \times 250 \times 1000 + 2100 + 1500}$$

(as 250 kVA
= power rating of
each transformer)

$$\gamma = 0.9952 = 99.52\%$$

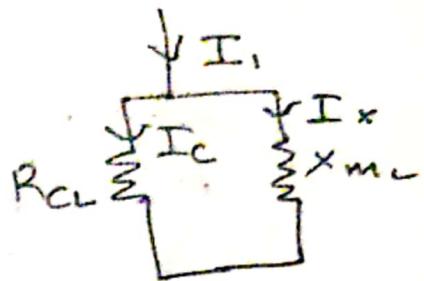

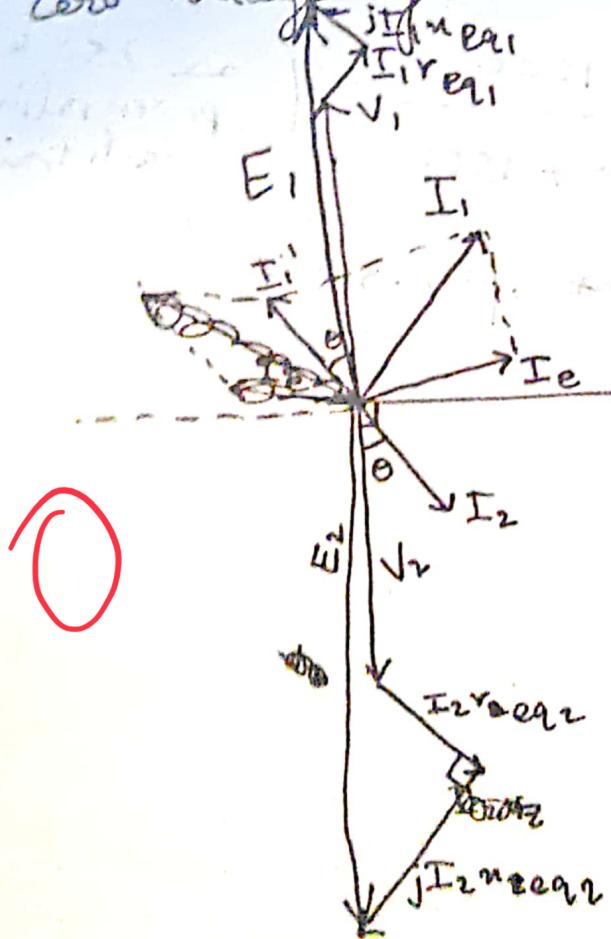4. Zero voltage regulation \rightarrow leading pf



$$\text{where, } \bar{I}_1 = \bar{I}'_1 + \bar{I}_e$$

$$E_2 = \bar{V}_2 + \bar{I}_2 (r_{eq2} + jx_{eq2})$$


and

$$E_1 = \bar{V}_1 + \bar{I}_1 (r_{eq1} + jx_{eq1})$$

$$\text{and } \tan \theta = \frac{r_{eq2}}{x_{eq2}}$$

where r_{eq2} and x_{eq2} are leakage components referred to secondary.

$$5] X = 100 \text{ kVA}$$

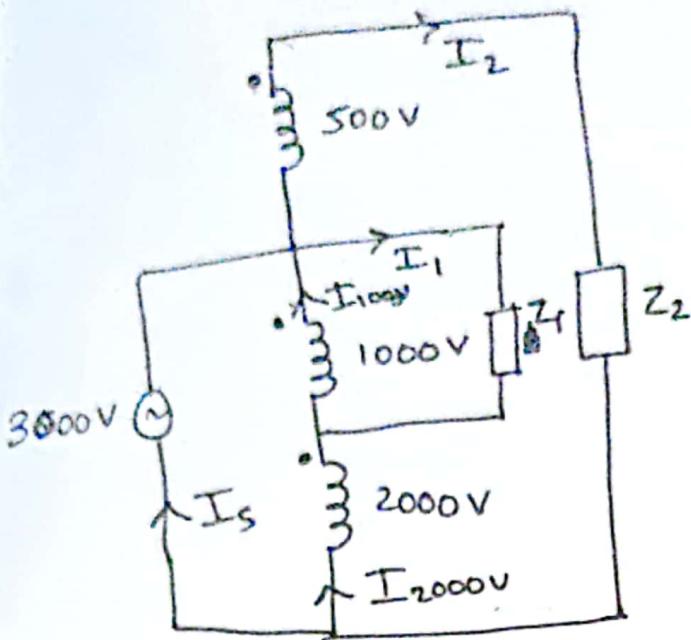

$$\begin{aligned} P_{Z_1} &= 130 + X \\ &= \frac{130}{230} \text{ kVA} \end{aligned}$$

$$\begin{aligned} P_{Z_2} &= 1000 + X \\ &= 1100 \text{ kVA} \end{aligned}$$

$$\therefore I_1 = \frac{P_{Z_1}}{1000 \text{ V}} = \frac{230 \times 10^3}{10^3} = \underline{\underline{230 \text{ A}}}$$

(3)

$$I_2 = \frac{P_{Z_2}}{\cancel{3500} \text{ V}} = \frac{\cancel{1100} \times 10^3}{\cancel{3500} \frac{10}{7}} = \underline{\underline{314.29 \text{ A}}} \quad \checkmark$$

Now, assuming efficiency of ~~of~~ autotransformer ≈ 1

$$\Rightarrow P_{\text{input}} = P_{\text{output}}$$

$$\Rightarrow 3000 \times I_s = P_{Z_1} + P_{Z_2}$$



$$\Rightarrow 3000 \times I_s = 1330 \times 10^3$$

$$I_s = \underline{\underline{443.33 \text{ A}}}$$

$$\begin{aligned} I_{1000 \text{ V}} &= I_2 + I_1 - I_s \\ &= 100.96 \text{ A} \end{aligned}$$

$$\begin{aligned} I_{2000 \text{ V}} &= I_s - I_2 \\ &= 129.04 \text{ A} \end{aligned}$$

$$6. \Phi = 7 \Rightarrow Y_d_7 ??$$

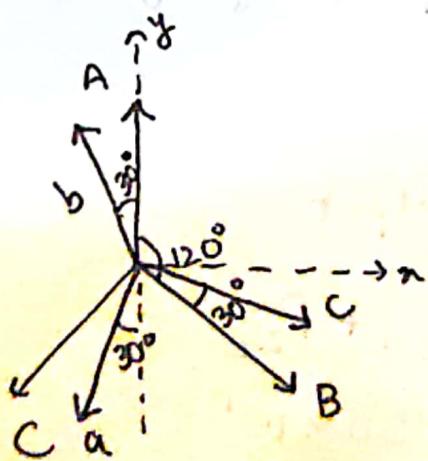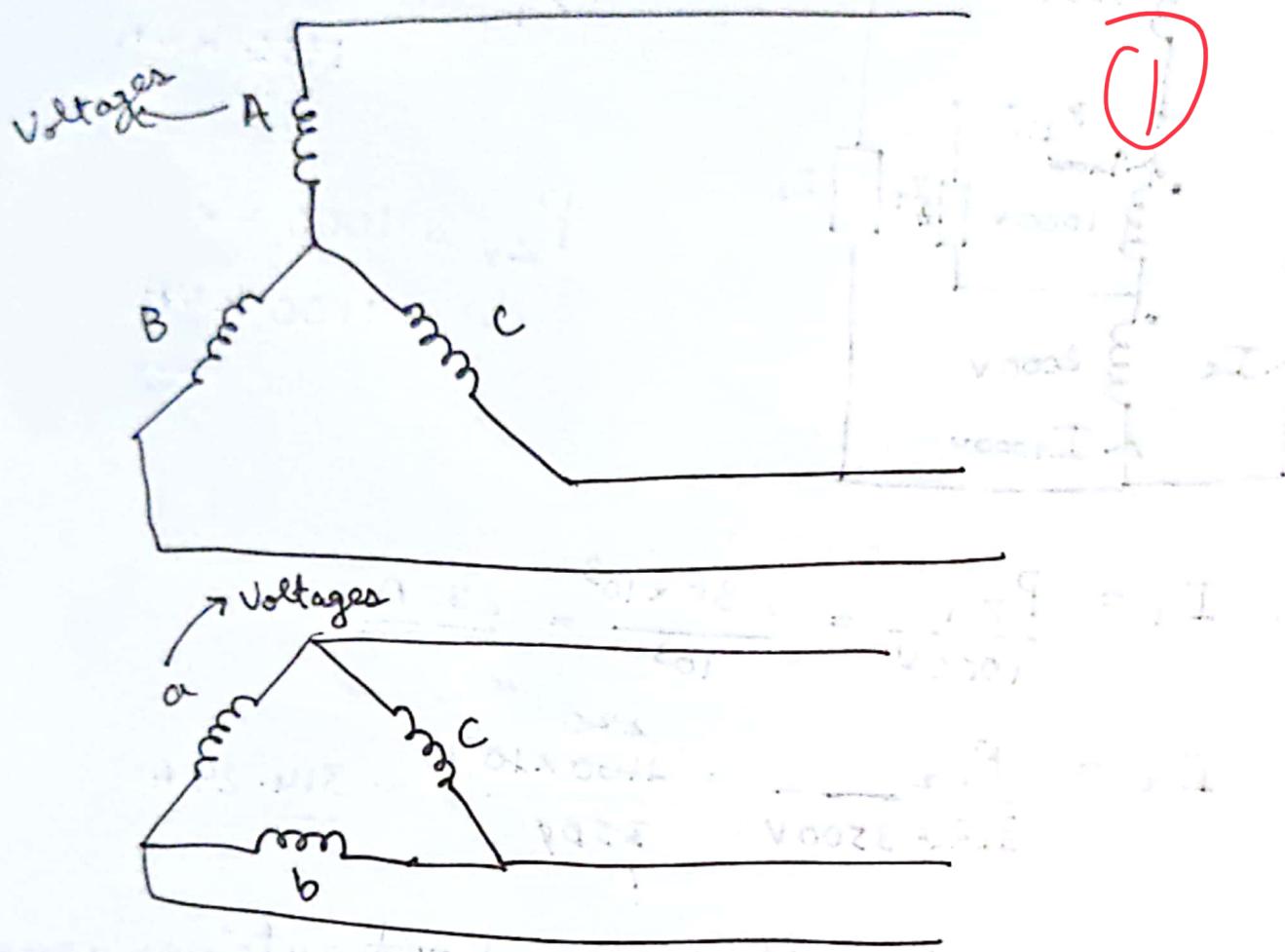

Phasor diagram

$\therefore a$ leads A by 150°
 b " B "
 c " " "